

# Circuits Discovery Sheet

The two most basic circuits are the parallel and series circuits. Can you design one of each?

Hints: use the squishy circuits dough in place of the wires.


Make sure you line up the positive and negative sides together.

Name:


Date:

Draw your circuit plan!

Parallel Circuit:

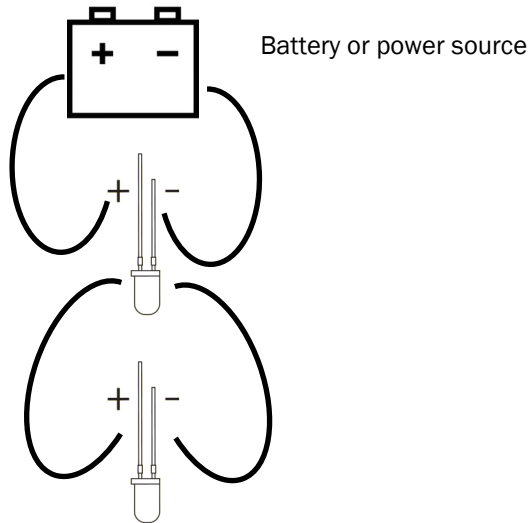


Series Circuit:

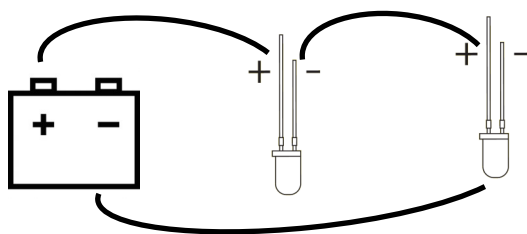

Draw your circuit plan!

SERIES

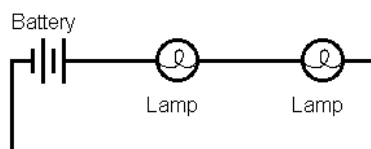

PARALLEL

